

## Electronic Communication Objective Questions and Answers Pdf

Question: 1

An oscillator is nothing but an amplifier with

- (A) Negative feedback
- (B) No feedback
- (C) Large gain
- (D) Positive feedback

Ans: D

Positive feedback

Question: 2

The unidirectional property of a pn-junction is useful for its use as a

- (A) Transformer
- (B) Amplifier
- (C) Oscillator
- (D) Rectifier

Ans: D

Rectifier

Question: 3

n-type of semiconductor is

- (A) Neutral
- (B) Negatively charged
- (C) Positively charged

(D) None of these

Ans: A

Neutral

Question: 4

The waves relevant to telecommunications are

- (A) Ultraviolet
- (B) Microwave
- (C) Visible light
- (D) Infrared

Ans: B

Microwave

Question: 5

The electrical circuits used to get smooth dc output from a rectified circuit is called

- (A) Amplifier
- (B) Full wave rectifier
- (C) Filter
- (D) Oscillator

Ans: C

Filter